

Homework Number 3

Telmen Enkhbold

San Francisco Bay University

1.

$$f = (A + \bar{C} + \bar{D})(\bar{B} + \bar{C} + D)(A + \bar{B} + \bar{C})$$

$$f = (Z + X)(\bar{Z} + \bar{Y})(\bar{Y} + X)$$

$$f = \overline{(X + Y)}Z + \bar{X}\bar{Y}\bar{Z}$$

4/

$$f = (A + \bar{C} + \bar{D})(\bar{B} + \bar{C} + D)(A + \bar{B} + \bar{C}) \quad (A, \bar{C}) \quad (\bar{B}, \bar{C})$$

Consensus theorem

$$f = (A + \bar{C})(\bar{B} + \bar{C})(A + \bar{B} + \bar{C}) \quad \text{distribute } (A + \bar{C}) \quad (\bar{B} + \bar{C})$$

$$f = (A\bar{B} + A\bar{C} + \bar{C}\bar{B} + \bar{C}) (A + \bar{B} + \bar{C})$$

$$f = (A\bar{B} + \bar{C})(A + \bar{B} + \bar{C})$$

$$f = A\bar{B}A + A\bar{B}\bar{C} + A\bar{B}C + \bar{C}A + \bar{C}\bar{B} + \bar{C}\bar{C}$$

$$f = A\bar{B} + A\bar{B} + AC + AC + \bar{C}\bar{B} + \bar{C}$$

$$f = A\bar{B} + AC + \bar{C}\bar{B} + \bar{C}$$

$$f = A\bar{B} + \bar{C}\bar{B} + \bar{C}$$

$$f = \bar{C} + \bar{B}$$

4/

$$f = (Z + X)(\bar{Z} + \bar{Y})(\bar{Y} + X)$$

$$f = (Z\bar{Z} + Z\bar{Y} + X\bar{Z} + X\bar{Y})(\bar{Y} + X)$$

$$f = (Z\bar{Y} + X\bar{Z} + X\bar{Y})(\bar{Y} + X)$$

$$f = (Z\bar{Y}\bar{Y} + Z\bar{Y}X + X\bar{Z}\bar{Y} + X\bar{Z}X + X\bar{Y}\bar{Y} + X\bar{Y}X)$$

$$f = (Z\bar{Y} + Z\bar{Y}X + X\bar{Z}\bar{Y} + X\bar{Z}X + X\bar{Y} + X\bar{Y}X)$$

$$f = (Z\bar{Y} + X\bar{Z}\bar{Y} + X\bar{Z}X + X\bar{Y} + Z\bar{Y})$$

$$f = (X\bar{Y} + X\bar{Z} + X\bar{Y} + Z\bar{Y})$$

$$f = X\bar{Y} + X\bar{Z} + Z\bar{Y}$$

3/

$$f = \overline{(X + Y)}Z + \bar{X}\bar{Y}\bar{Z}$$

$$f = \bar{X}\bar{Y}Z + \bar{X}\bar{Y}\bar{Z}$$

$$f = \bar{X}\bar{Y}(Z + \bar{Z})$$

$$f = \bar{X}\bar{Y}$$

2.

### Adder-Subtractor Operation:

1. **Full Adders (FA):** There are four full adder (FA) blocks in the circuit. Each full adder takes in three inputs: two bits from the numbers **A** and **X** to be added and a carry input from the previous stage. It outputs a sum **S** and a carry **C**.
2. **Add/Subtract Control (S):** The control input **S** determines whether the circuit performs addition or subtraction.
  - If **S=0**: The circuit adds the numbers **A** and **B**.
  - If **S=1**: The circuit subtracts **B** from **A**.
3. **XOR Gates:** The XOR gates (with inputs **B** and **S**) are used to determine the value of **X** based on **B** and the control signal **S**.

### Implementation:

1. **When S=0 (Addition)**
  - **X** is equal to **B**, meaning  $X_i = B_i$ .
  - **C<sub>0</sub>** (initial carry) is set to **0**.
  - The circuit adds **A** and **B**.
2. **When S=1 (Subtraction)**
  - **X** is the bitwise NOT of **B**, meaning  $X_i = \bar{B}_i$ .
  - **C<sub>0</sub>** (initial carry) is set to **1**.
  - This operation effectively adds **A** to the two's complement of **B**, performing subtraction.

### Test Cases:

1.  $A + B = 7 + (-3) = 4$

- Convert the numbers to 4-bit binary: A (7) = 0111 B (-3) = 2's complement of 3 = 1101
- Set  $S = 0$  for addition: The circuit adds  $0111 + 1101 = 10100$ . The result is 0100 (4 in decimal) with an overflow.

2.  $A - B = -6 - (-1) = -5$

- Convert the numbers to 4-bit binary: A (-6) = 2's complement of 6 = 1010 B (-1) = 2's complement of 1 = 1111
- Set  $S = 1$  for subtraction: The circuit adds  $1010 + 0001$  (because of two's complement) = 1011. The result is 1011 (-5 in decimal when interpreted as two's complement).

3.

1.

Load 104

Opcode - 0001

Int - 104, Hex - 68, Binary - 1000100, 12 bits - 0001 000100

Machine Code - 0010 0001 000101

2.

Add 105

Opcode - 0010

Int - 105, Hex - 69, Binary - 1000101, 12 bits - 0001 000101

Machine Code - 0010 0001 000101

3.

Store 106

Opcode – 0011

Int - 106, Hex – 6A, Binary – 1001010, 12 bits – 0001 001010

Machine Code – 0011 0001 001010

4.

Halt

Opcode – 0100

Machine Code – 0100 0000 000000